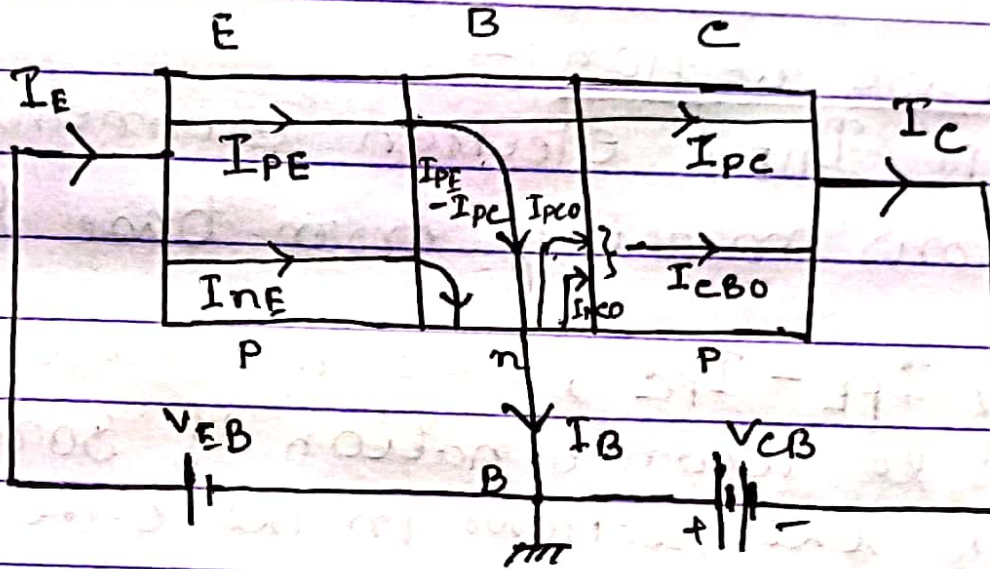


Transistor

PNP \rightarrow current components

pioneerpaper.co
Page: 15/03/2020
Date: 24/03/2020

CB mode:-



Transistor current component of a PNP transistor with emitter junction is forward biased and collector junction is reverse biased. are shown in figure.

In emitter region:

(1) I_{PE} , hole current density due to holes moving from emitter to base.

(2) I_{NE} , electron current due to electrons moving from base to emitter.

Therefore, emitter current

$$I_E = I_{PE} + I_{NE} \quad \text{--- (1)}$$

In base region:-

(i) I_{NE} , electron current due to electrons moving from base to emitter.

(ii) $I_{PE} - I_{PC}$, recombination current due to recombination of some holes with the electrons in the base region.

(iii) $I_{CBO} = I_{PCO} + I_{NCO}$, leakage current, as the collector junction is reverse bias, we get a current due to drift of minority carriers.

$I_{PCO} \rightarrow$ due to holes from base to collector

$I_{NCO} \rightarrow$ due to electrons from collector to base.

Therefore, base current

$$I_B = I_{NE} + (I_{PE} - I_{PC}) - I_{CBO} \quad \text{--- (2)}$$

In collector region:-

(i) I_{pc} , hole current, some of the holes recombine at the base region and maximum number moved to the collector region.

$$(ii) I_{cBO} = I_{pcO} + I_{ncO} ,$$

Therefore, collector current,

$$I_c = I_{pc} + I_{cBO}$$

(3)

combining equation (1), (2) and (3)
we get

$$I_B + I_c = I_{nE} + I_{pE} - \cancel{I_{pc}} - \cancel{I_{cBO}} + \cancel{I_{pc}} + \cancel{I_{cBO}}$$

Since,

$$I_{nE} + I_{pE} = I_E$$

$$\therefore I_B + I_c = I_E$$

Current gain of a transistor:- (α and β)

① α -of a transistor:- In common base configuration, the d.c. current gain of a transistor is denoted as ' α ', which is defined as the ratio of the collector current to the emitter current

i.e
$$\alpha = \frac{I_c}{I_E} \text{ Without leakage current}$$

$$\alpha = \frac{I_c - I_{CBO}}{I_E} \text{ With leakage current}$$

In common base configuration, the a.c. current gain is denoted by α_{ac} , which is defined as the ratio of the change in collector current to the change in emitter current

i.e
$$\alpha_{ac} = \frac{\Delta I_c}{\Delta I_E}$$

For a good transistor $\alpha_{ac} = \alpha_{dc} = \alpha$

α -value lies betⁿ 0.98 to 0.99

(2) β of a transistor: - In Common emitter Configuration, the d.c current gain of a transistor is denoted by β , which is defined as the ratio of the collector to the base current.

$$\text{i.e. } \beta = \frac{I_c}{I_B} \text{ without leakage current}$$

$$\beta = \frac{I_c - I_{CBO}}{I_B} \text{ with leakage current}$$

In Common emitter Configuration, the a.c current gain is denoted by β_{ac} , which is defined as the ratio of the change in collector current to the change in base current.

$$\text{i.e. } \beta_{ac} = \frac{\Delta I_c}{\Delta I_B} \text{ for a}$$

For a good transistor, $\beta_{dc} = \beta_{ac} = \beta$

Remember β of a transistor lies bet
22 to 200

(in general)

Relation betⁿ α and β :-

We have $I_E = I_B + I_C$

or $\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$

or $\frac{1}{\alpha} = \frac{1}{\beta} + 1$

or $\alpha = \frac{\beta}{\beta + 1}$

or $\beta = \frac{\alpha}{1 - \alpha}$

* Different Relation of collector current in terms of leakage current :-

Relation -1
 I_C in term of α (Common base configuration)

We have, $\alpha = \frac{I_C - I_{CBO}}{I_E}$

where I_{CBO} = leakage current in CB mode.

or $I_C = \alpha I_E + I_{CBO}$

~~also~~ also

$$\alpha I_E = I_C - I_{CBO}$$

$$\text{or } \alpha (I_B + I_C) = I_C - I_{CBO}$$

$$\text{or } I_C (\alpha - 1) = -\alpha I_B - I_{CBO}$$

$$\text{or } I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

Also $\alpha = \frac{\beta}{1+\beta}$ Thus $\frac{\alpha}{1-\alpha} = \beta$ and

⊗ $\frac{1}{1-\alpha} = (\beta+1)$

Thus $I_C = \beta I_B + (\beta+1) I_{CBO}$

Relation-2 I_c in terms of β

(common emitter mode)

$$\text{we have, } \beta = \frac{I_c - I_{CE0}}{I_B}$$

where $I_{CE0} \rightarrow$ leakage current in CE mode.

$$I_c = \beta I_B + I_{CE0}$$

Relation-3

Relation betⁿ two leakage current
i.e. $I_{CBO} = (\beta + 1) I_{CBO}$

current gain with leakage in c-b mode.

$$\alpha = \frac{I_c - I_{CBO}}{I_E}$$

$$\Rightarrow \alpha I_E = I_c - I_{CBO}$$

$$\Rightarrow \alpha (I_B + I_c) = I_c - I_{CBO}$$

$$\Rightarrow I_c = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$\Rightarrow I_c = \beta I_B + (\beta + 1) I_{CBO} \quad \text{--- (7)}$$

current gain with leakage in CE mode.

$$\beta = \frac{I_c - I_{CE0}}{I_B}$$

$$I_C = \beta I_B + I_{CE0} \quad \text{--- (2)}$$

Comparing eqⁿ (1) and (2) we get

$$I_{CE0} = (\beta + 1) I_{CB0}$$